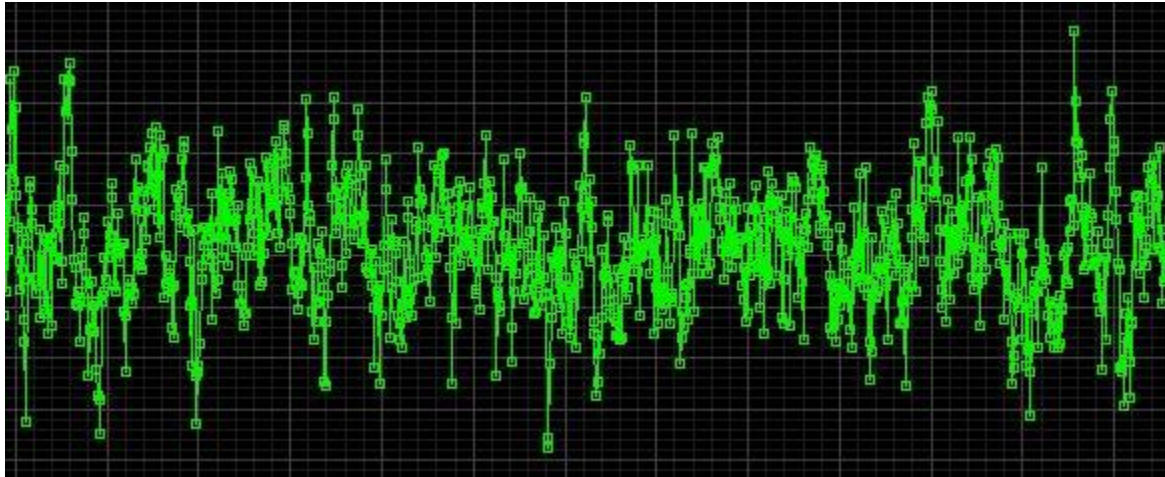


Noise limitations in SCA.

eric.delagnes@cea.fr





Relation between noise & jitter.

$$\sigma_t = \sigma_V \cdot dV/dt$$

“Low” frequency noise can be rejected digitally
(baseline subtraction, digital filter, digital CFD...)

dV/dt is proportional to A/BW

  

$$\sigma_V^2 = G(\sigma_D^2 + 2\sigma_G^2) + \sigma_{SCAin}^2 + \sigma_{SCAout}^2 + \sigma_{ADC}^2$$

$$A(t) = G \cdot S(t)$$

- σ_D and σ_G are the contribution of detector + amplifiers: scales as $BW^{1/2}$.
- σ_{SCA} contribution of the SCA
 - σ_{SCAin} part scales as $BW_{SCAin}^{1/2}$.
 - σ_{SCAout} (after the sampling) is independent of BW_{SCAin}
- σ_{ADC} digitization noise (including quantization noise ($LSB/12^{1/2}$)).

« 2nd
Stage »



Switches in scaled down technologies.

- MOS switch Ron resistance given by :

$$R_{ON} \approx \frac{1}{g_{ds}} = \frac{1}{\mu * C_{ox} \frac{W}{L} (V_{gs} - V_{th})}$$

Highly non linear


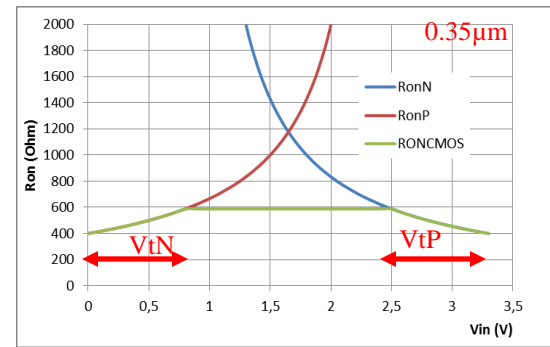
 
- Usually it is linearized by using NMOS & PMOS in parallel and swing set to $\sim V_{DD}/2$



- In advanced technologies:

V_{DD} is reduced, V_{TH} also but not in the same ratio \Rightarrow max signal decrease.

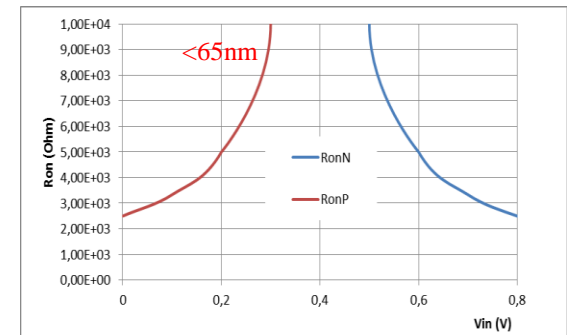 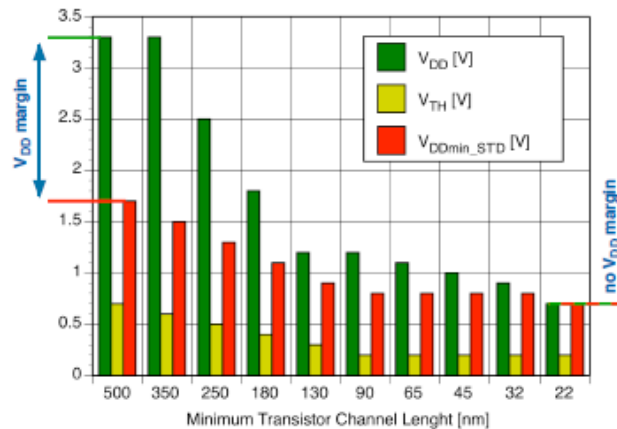CMOS switches linear region is smaller & smaller




Max signal decreasing with technology scaling.

- In advanced technologies:

- CMOS switch less useful => use of NMOS only switch. Swing now centered near gnd.
=> can be a good thing as PMOS switches (3 x larger than NMOS switches) are heavily loading the input SCA input (lumped RC on the input bus)

- But R_{on} now vary a lot with V_{in} : => BW vary with V_{in}
=> Distorsion => poor ENOB

© Baschirotto

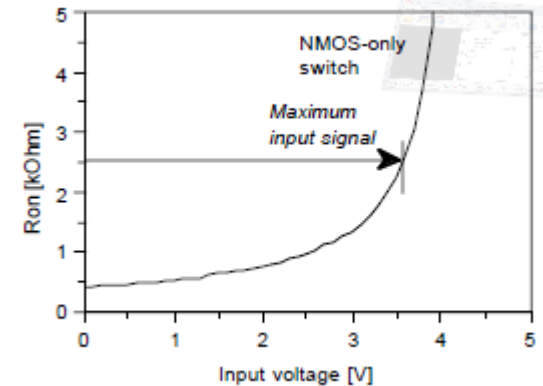


- Solutions (can be cumulative):

- Limit the input swing to stay in the linear region.
- On-chip clock multiplication
- Bootstrapped switch ($V_{GS}-V_T = cte$) used in modern ADCs.

Need for extra capa on the input bus. Feasible in a SCA ?

© Baschirotto

 


- Differential input : swing multiplied by 2. Effect of non constant R_{on} averaged.


In any case A reduced => need some effort on σ_v to get a good time resolution.

Noise source in SCAs

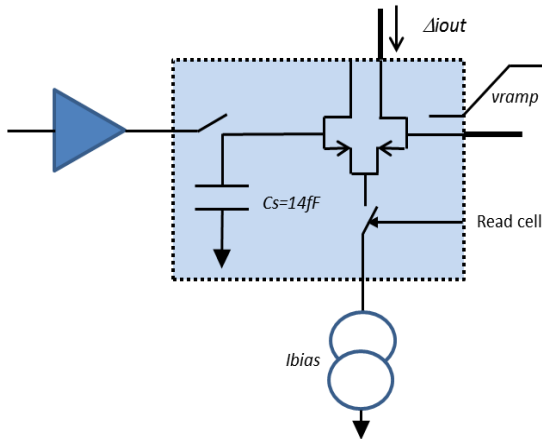
- Very architecture dependent . 3 family of designs studied:



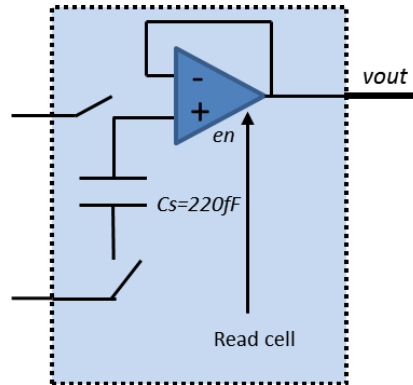A la Target:
Buffered SH
Wilkinson Readout
Very Small Cs



 A la DRS:
Unbuffered diff SH
Closed Loop Follower
readout.



A la SAM:
Buffered SH
Fed Back OPAMP readout
Fully differential

- But Common features/rules are existing.
- 4 kinds of “noise” can be distinguished:
 - The noise due to artefacts.
 - The pickup noise / D->A coupling / Power supply noise
 - “Dynamic” noise : distorsion, non linearities...
 - The intrinsic electronic noise : the most easy to understand and to manage

Noise due to artefacts.

- Unwanted behavior of the digital part : metastability ...
- Ghost pulses : the old events are not fully erased before a new is written in the SCA
 - ⇒ memory of a previous pulse.
 - ⇒ Dielectric absorption problems reported in the SCA of early 90s.
- XTALK in some special cases (mixing of signal with very different amplitudes, saturation).
- Coupling between input and output
 - ⇒ All the high impedance nodes of the SCA are perfect receivers (capacitive coupling) for the high frequency input signals.
 - ⇒ The output impedance of a closed loop OTA is high at high frequency.
- In the following slides we assume that some “fix pattern” spread (offset, gain) can be corrected offline
 - ⇒ valid only if stable (with time, temperature...):
 - ⇒ More stable if closed loop or differential structures
 - ⇒ If not, they are randomized and are contributing to noise.

Noise due to couplings : may affect operation during sampling or readout


- On and off chip D->A coupling:
 - Very dependent on layout, technology and substrates.
 - In SCAs, we are obviously in very favorable situation :
 - No gain in intrinsic part of the SCAs (excepted the hidden ones).
 - Any idea of what happens when $\times 10$ or 20 gain integrated in the chip ?
- Minimize high impedance nodes.
- Larger Cs => Larger robustness
- The couplings which are synchronous with the sampling clock (or dividers) are often reproducible and may be seen as “pedestals”.
- Avoid asynchronous clocks or asynchronous signal dispatched everywhere.
- Differential signaling helps a lot (If CMR still exists @ HF)

Noise from power supplies

- External noise (ie from DC-DC converters).
- Noise can be generated by outside digital logic or by the activity of the chip itself
- Sensitivity to the power supplies (PSRR):
 - Closed loop structure are more robust (esp. if using OPA), but very scales as open loop gain.
 - Differential operation helps a lot.
 - Worst when VDD is smaller.

Dynamic « noise »

 
- Dynamic distortion of the signal may be seen as noise.
 - Systematic non linearities:
 - Switches(Q injection), amplifiers: can eventually be calibrated and corrected.
 - Bandwidth dependency:
 - along the SCA (bus resistances): problem for long SCAs.
 - With the amplitude:
 - Switch non linearities (R_{on})
 - Slew rate.
 - Dependency of the sampling time with the signal level.




IN ADC datasheets: all this is included in the ENOB (together with jitter)

Intrinsic Noise in SCAs

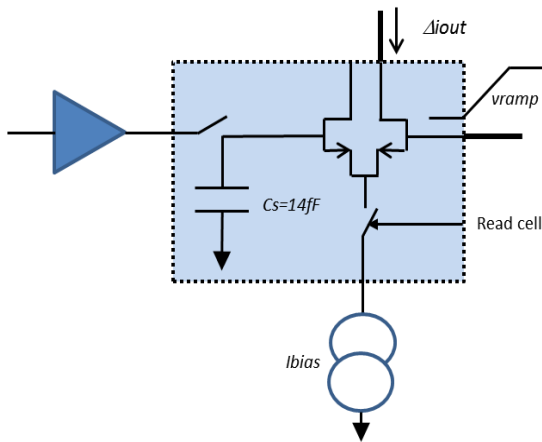
- Very architecture dependent
- 3 very different designs developed in the community
- But Common features/rules are existing.



 « Target »:
Buffered SH
Wilkinson Readout
Very Small Cs




 « DRS »:
Unbuffered diff SH
Closed Loop Follower
readout.



« SAM »:
Buffered SH
Flip around readout
Fully differential

 kTC or sampling noise when switching with MOS



When integrating the noise over the noise BW:

$$\Rightarrow \langle V_s \rangle^2 = 4 \cdot \gamma \cdot k \cdot T \cdot R_{on} \cdot B_N \text{ if } 1/f \text{ is neglected}$$


With Noise Bandwidth $B_N = \pi/2 \text{ BW} = 1/(4 \cdot R_{ON} \cdot C_s)$

$$\Rightarrow \langle V_s \rangle^2 = \gamma \cdot k \cdot T / C \text{ sampled on } C_s$$

It is often reduced to kT/C

$1/f$ noise contribution very complicated, mainly independant on C_s and often neglected . Is it still true for deep submicron ?

Noise in CMOS technologies

 

When referred to input

en: Noise spectral density
$$e_n^2 = \frac{4kT\gamma}{g_m} + \frac{K_F}{C_{gs}f}$$

Thermal noise:
 γ = non ideality factor $\geq 2/3$
 g_m : transconductance scales as:
 W/L and $I_D^{1/2}$ in strong inversion
 I_D in weak inversion

Flicker Noise: main source @ low frequency
 ~ independent of I_D
 Scales as (area)-1
 Extends to few MHz in modern CMOS



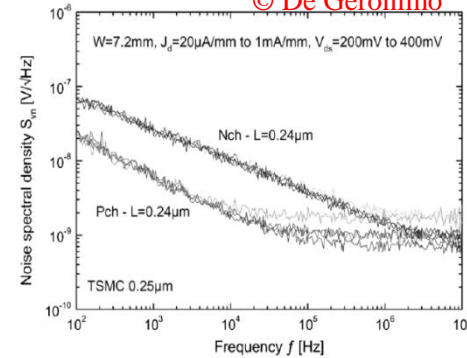


Fig. 12. Measured equivalent input noise spectra for n- and p-channel devices with minimum L and different J_D in TSMC 0.25 μm.

Effect of Technology scaling

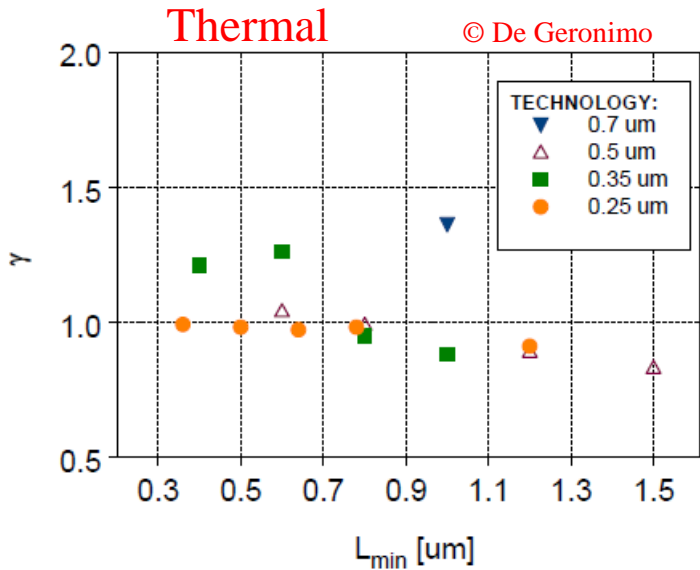

 No dramatic degradation of γ with scale down



- High dependence with process details
- larger K_f when scaling down
- Degradation in time reported.

Intrinsic SCA Electronics noise: Quadratic sum of 4 terms

- **Input Buffer noise (if exists):**

- $\sigma_{\text{BUF}} = e_n \cdot (\pi/2 \text{ OBW})^{1/2}$

- e_n is the noise voltage density of the input pair, scales as $g_m^{1/2}$ ie $I_d^{-1/4}$

- $\sigma_{\text{BUF}} = 150 \mu\text{V rms} / 450 \text{MHz BW}$ in SAMLONG ($e_n = 4 \text{nV} / \sqrt{\text{Hz}}$)

- **Sampling noise** $\sigma_{\text{kTC}} = (kT/C_S)^{1/2} = \text{noise floor of the SCA.}$

=> obvious tradeoff between noise and BW

| | Target | DRS4 | SAM(LONG) |
|---|--------|------|-----------|
| Cs (fF) | 14 | 250 | 300 |
| σ_{kTC} ($\mu\text{V rms}$) | 540 | 130 | 120 |

- **Output Mux or output buffer (if exists):**

- Mainly OPAMP used as voltage follower.




- Scales as $1/\sqrt{g_m} = I_d^{-1/4}$ and as $(\text{OBW})^{1/2}$ (output BW, can be decreased if lower speed readout).

- $80 \mu\text{V rms}$ in SAMLONG (20MHz multiplexing).

- **Readout noise.** See next slide.

ALL THESE CONTRIBUTIONS ARE MULTIPLIED BY 2 fo diff. operation.

SCA ReadOut Noise: Wilkinson Readout

   

- Ramp noise**

$$\sigma_{Ramp}^2 = (i_n^2/2 \cdot t + K^2 K_f \cdot t^2) / C_r^2$$

i_n^2 is the thermal noise density of the current source
(scales as gm or $I_{ramp}^{1/2}$)

K_f is the flicker noise coefficient, K is a constant.


⇒ Fast conversion is favorable.

⇒ Sigma scales as $1/C_r^{3/4}$ (thermal) or $1/C_r$ (1/f)

- Comparator noise.**

Highly depend on the structure.

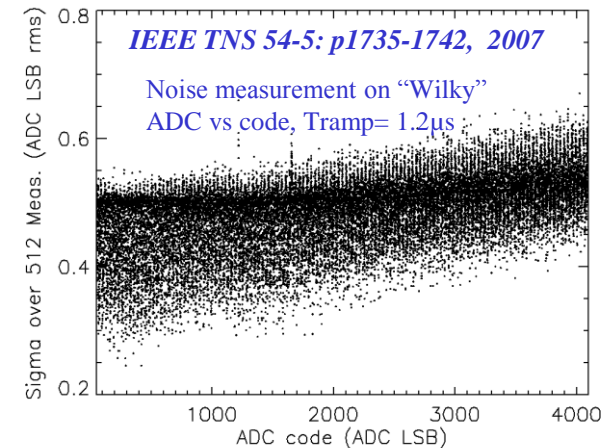For a given speed σ_{comp}^2 scales as $1/gm$ of the input pair.



SCA ReadOut Noise: Follower readout


- Unity gain OTA or OPA

If well designed (negligible 2nd stage noise).

$$\sigma_{Fol} = e_n \cdot (\pi/2 \text{ OBW})^{1/2}$$

with e_n scaling as $1/\sqrt{g_m}$ (ie $1/ID^{1/4}$) and $1/(W/L)^{1/2}$ of the input MOS pair
one OTA/cell => transistor size limited

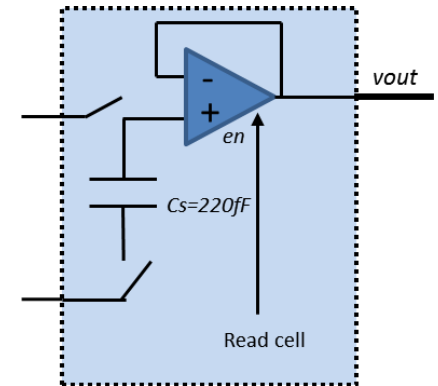- If not set externally OBW is proportional to g_m / C_c
 $\Rightarrow \sigma_{Fol}$ becomes independent on g_m
- If set externally: this contribution can be decreased if the RO frequency is decreased.
- For the same power consumption the noise of a MOS used as a source follower is better by 2 or more (for the same area used).



SCA ReadOut Noise: Flip around Readout

Unfortunately this configuration amplify the OPAMP noise:

$$\sigma_{FA1} = e_n \cdot (C_p + C_s / C_s) \cdot (\pi/2 \text{ OBW})^{1/2}$$


With e_n = input refered noise density of the amplifier
scales as 1/gm.

can be minimized by increasing input transistor size (only one ampli/ channel)

=> C_p must be minimized by design/layout and C_s maximized.

=> for long SCA the noise becomes proportional to the SCA length.

 => can be decreased if OBW is limited => slower readout.




Before reading C_s , C_p must be reset:

=> extra contribution $\sigma_{FA2} = (kT/C_s)^{1/2}$ with the most efficient reset scheme

On SAMLONG RO noise contribution is $\sigma_{FA1} = 270\mu\text{V rms}$ (20MHz ReadOut)

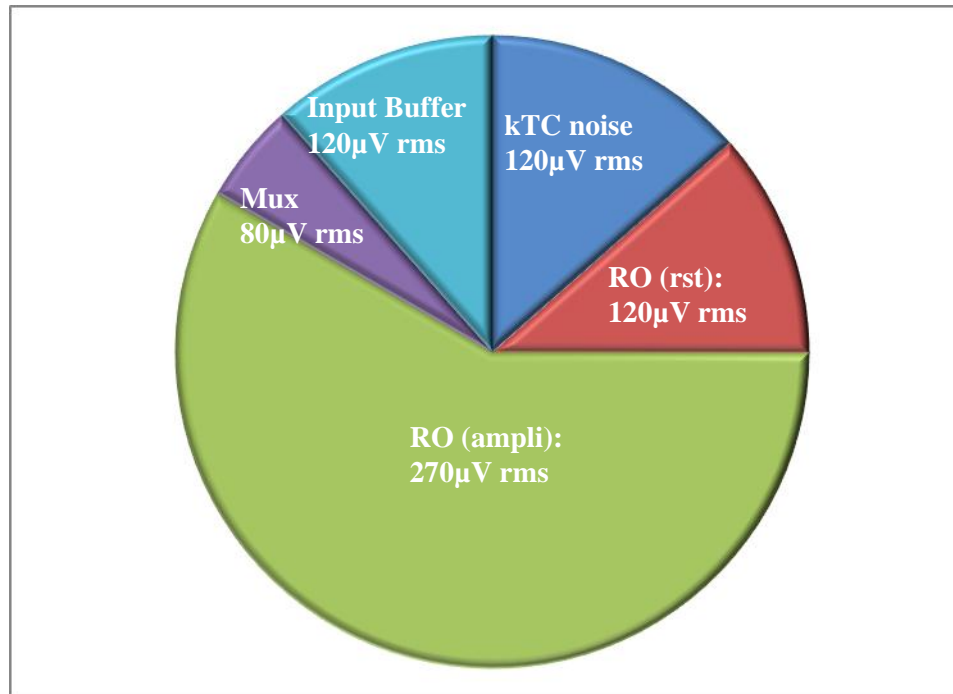Exemple: of the « Intrinsic Noise » contributions for SAMLONG




Total : 350µV (single ended) => 500µV rms differential

**Clearly dominated by ReadOut contribution:
Price to pay for a “robust” readout.**


Another possible noise contribution

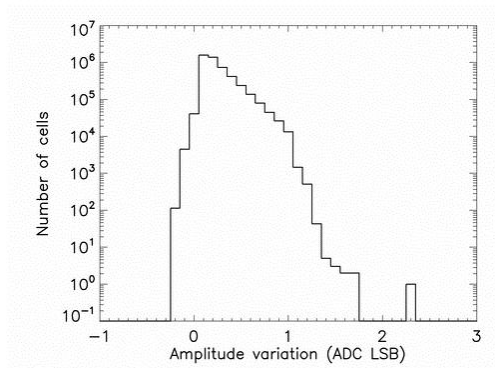- Switches Leakage currents are discharging Cs:
=> voltage drop depending on time between W and R.
- Not an issue with old technologies:




AFTER Chip (T2K TPC) AMS 0.35 μm
Distribution of the voltage on 120 chips * 65000 cells
drop after 2 ms.
1 LSB = 0.5mV => 55fA

 - Can become a problem in deep submicron:



Gate tunneling current

 

Low V_T + Low weak inversion slope

Use of True Differential signaling ?

- Pros:

- Max signal doubled.
- SCA noise increased by $\sqrt{2}$
- Less distortion (even harmonics cancelled)
- D/A coupling rejected
- Good PSRR
- Leakage effect compensation.
- **Massively adopted in industry**

} S/N increased by $\sqrt{2}$

- Cons:

- Power consumption increase.
- SCA surface doubled.
- With a similar increase, you could increase Cs and theoretically improve the S/N by more than $\sqrt{2}$
- Detector signal are often single ended => need for an interface element

Use of OPAMP or single-ended structure ?

- In the first fast SCA we designed (ARS):
 - The amplifiers were single ended.
 - The structure was not differential.
- REAL S/N was limited to ~8-9 bits because of temperature stability of gain and baseline spread (no correction performed at all)
 - => All this has been improved by the use of closed loop OPAMP.
- But for the same power consumption, the noise of an OPAMP is more than $\sqrt{2}$ larger than for a single ended one.
- Modern technologies are offering NMOS with separate wells
 - => Good candidates for linear followers, power , area and speed efficient.
 - => Used in the MDACs of several recently published 10-bit pipeline ADC designs.
 - => Differential structure cancels spread and sensitivity to supplies and temperature .



**THANK YOU FOR
YOUR ATTENTION**